

## **Single/Dual BDC motor system for medium current applications**

This document shares the tests results of the DRV8816 EVM with a Anaheim Automation BDC motor (BDD-38-63-12.0V-14200). The testing is performed with default firmware loaded into the MSP430G2131. This test data further enables the end user to familiarize the operations in medium current ( 0.3A-2.5A) applications.

The data is structured into 4 main categories.

1. Single Motor Bi Directional Control
2. Current Proportional output range.
3. Motor Voltage vs RPM
4. Thermal Image of device under operations.

### **Section 1:**

Single motor is connected between OUT1 and OUT2 .


The data demonstrates the motor current behavior at the OUT 1 and OUT 2 of the motor terminal when the motor is commanded FORWARD and REVERSE as per the following table. The duty cycle is varied by changing the potentiometer .

EN1	EN2	IN1	IN2	OUT1	OUT2	Operation
1	1	1	0	H	L	Forward
1	1	0	1	L	H	Reverse


Note: The device is not commanded into BRAKE mode for this experiment.

## Forward Motor Motion (FWD )

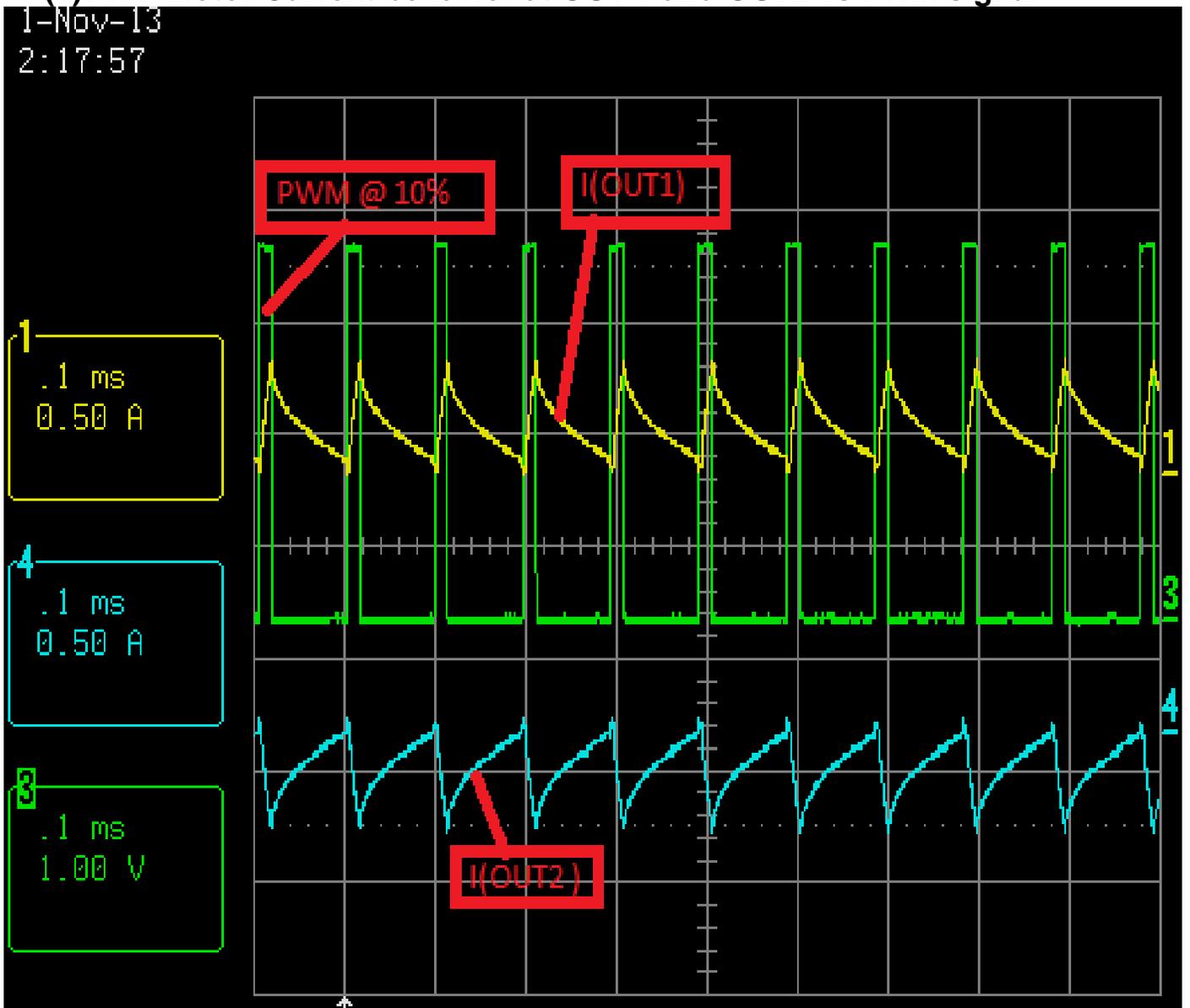
### (1)FWD-Motor Current behavior at OUT 1 and OUT2 vs PWM signal


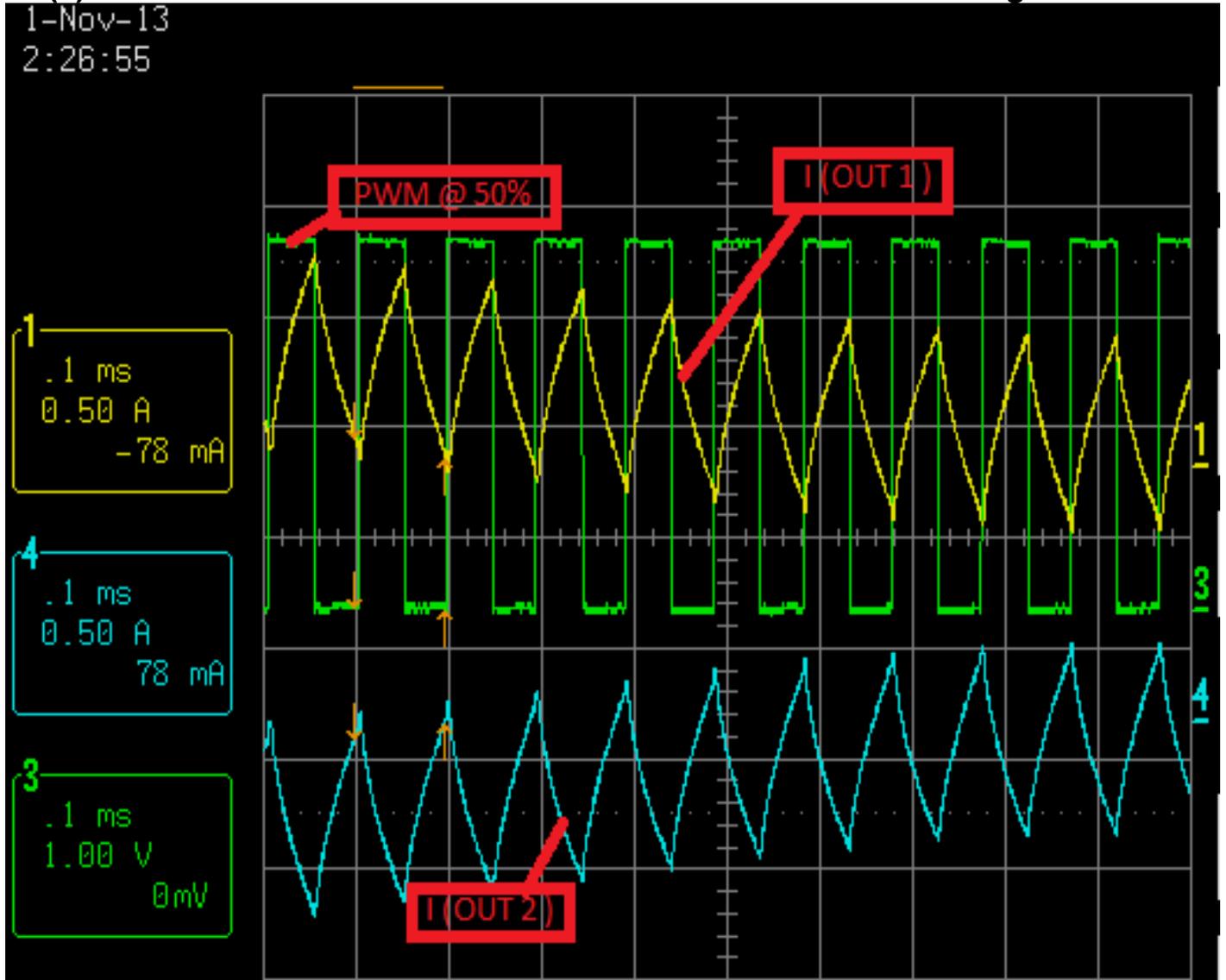
## (2) FWD- Motor Current behavior at OUT 1 and OUT2 vs PWM signal



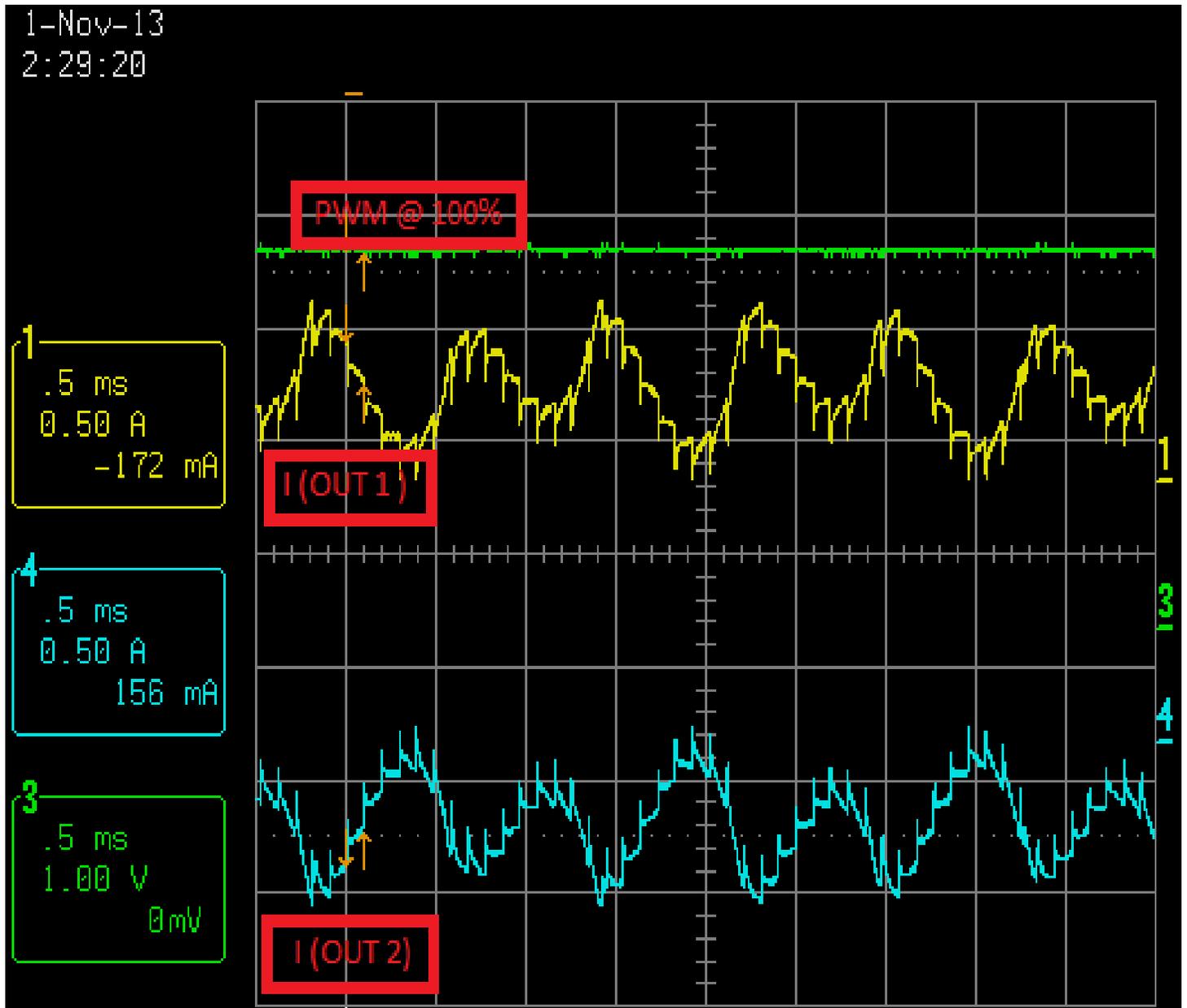
### (3) FWD-Motor Current behavior at OUT 1 and OUT2 vs PWM




## Reverse Motor Motion (REV )

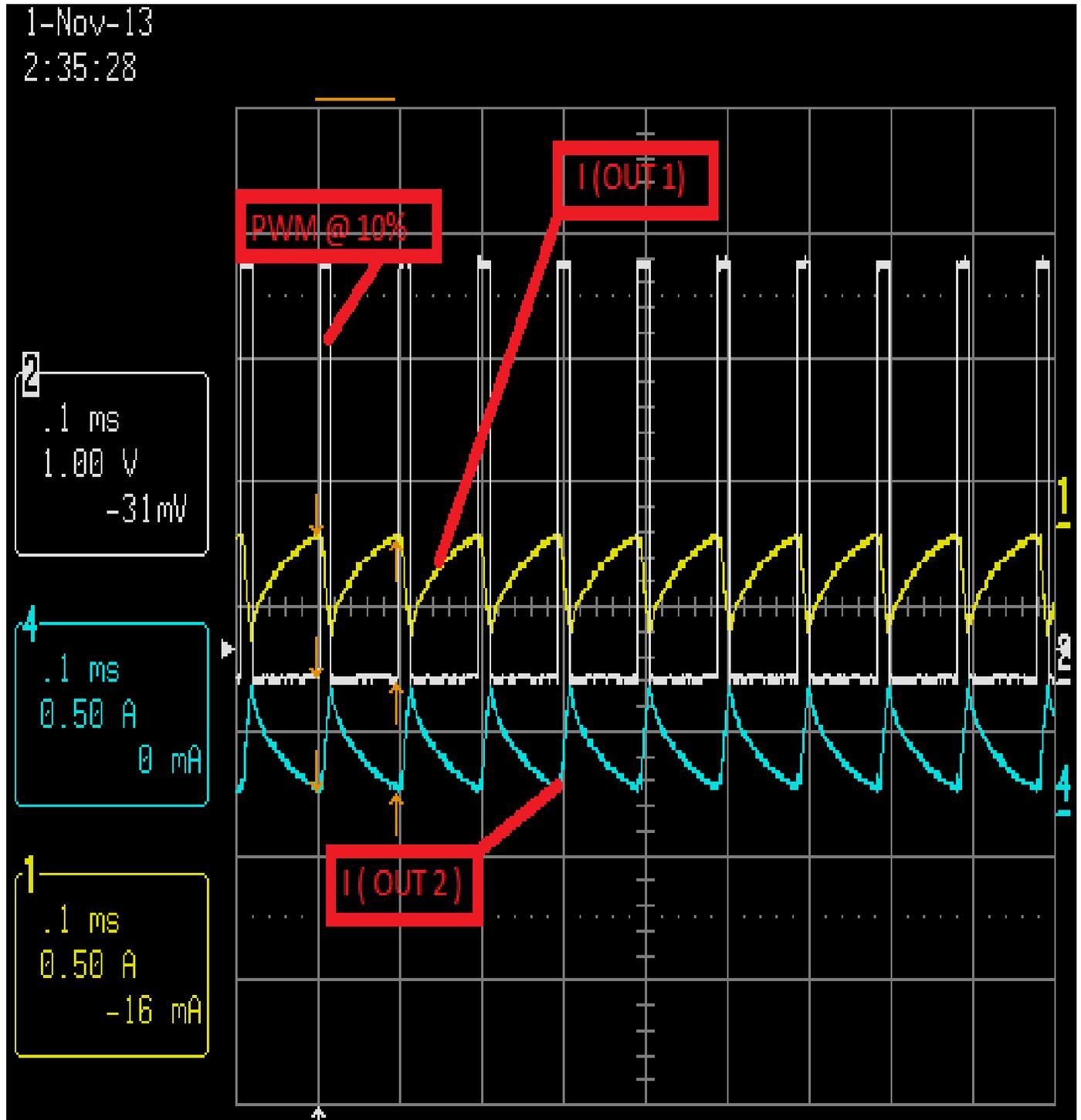
(1)REV-Motor Current behavior at OUT 1 and OUT2 vs PWM signal


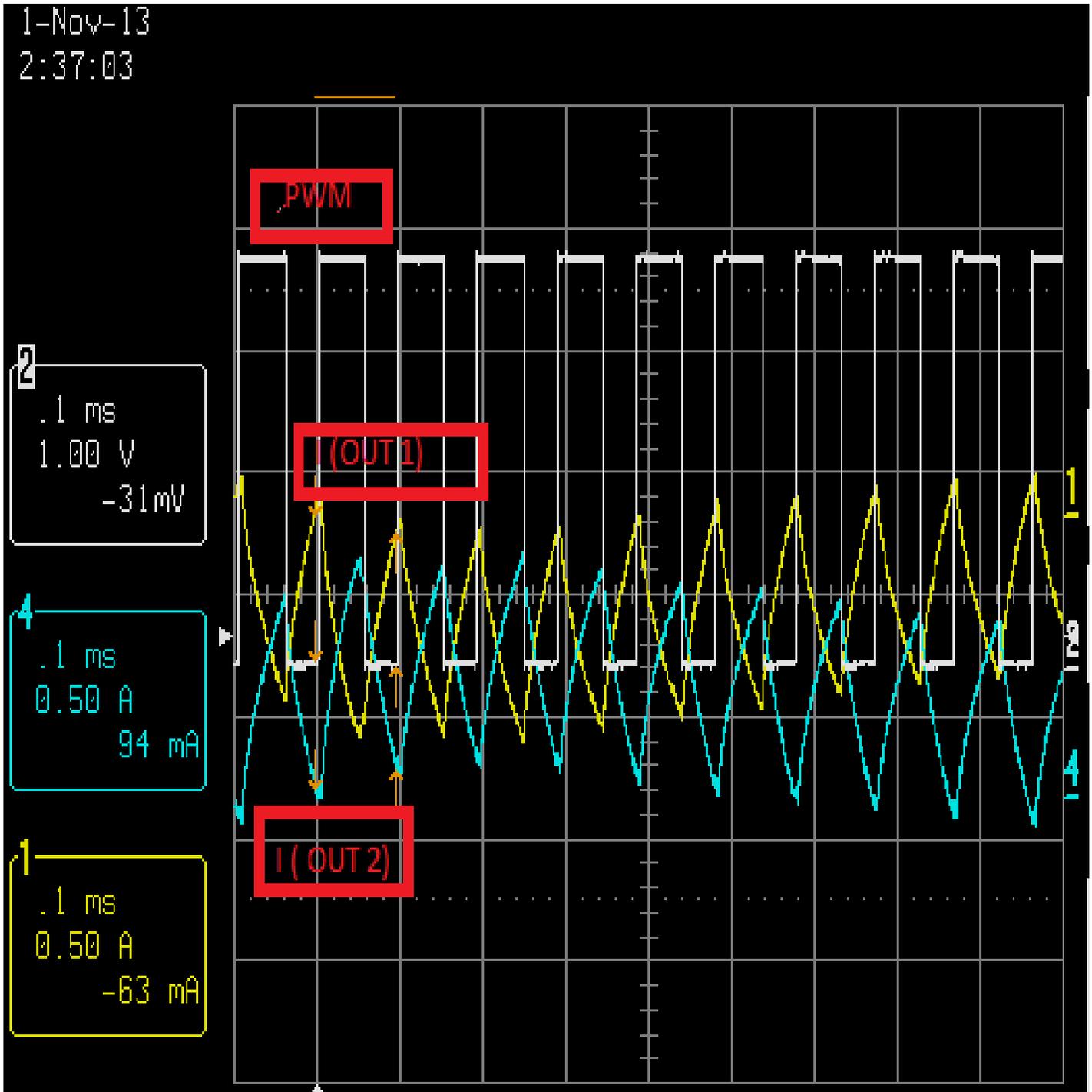
## (2)REV-Motor Current behavior at OUT 1 and OUT2 vs PWM signal



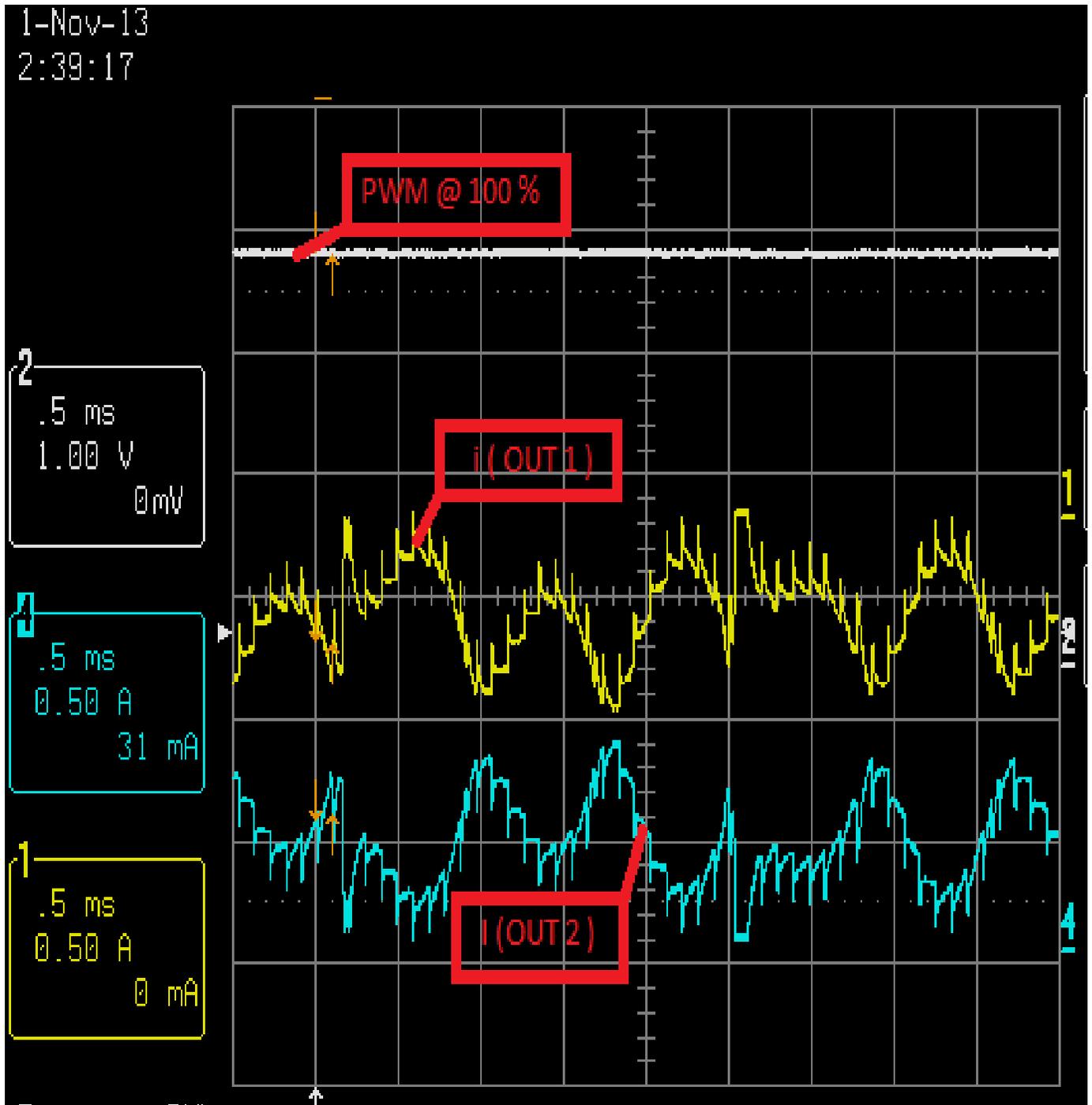
### (3)REV-Motor Current behavior at OUT 1 and OUT2 vs PWM signal


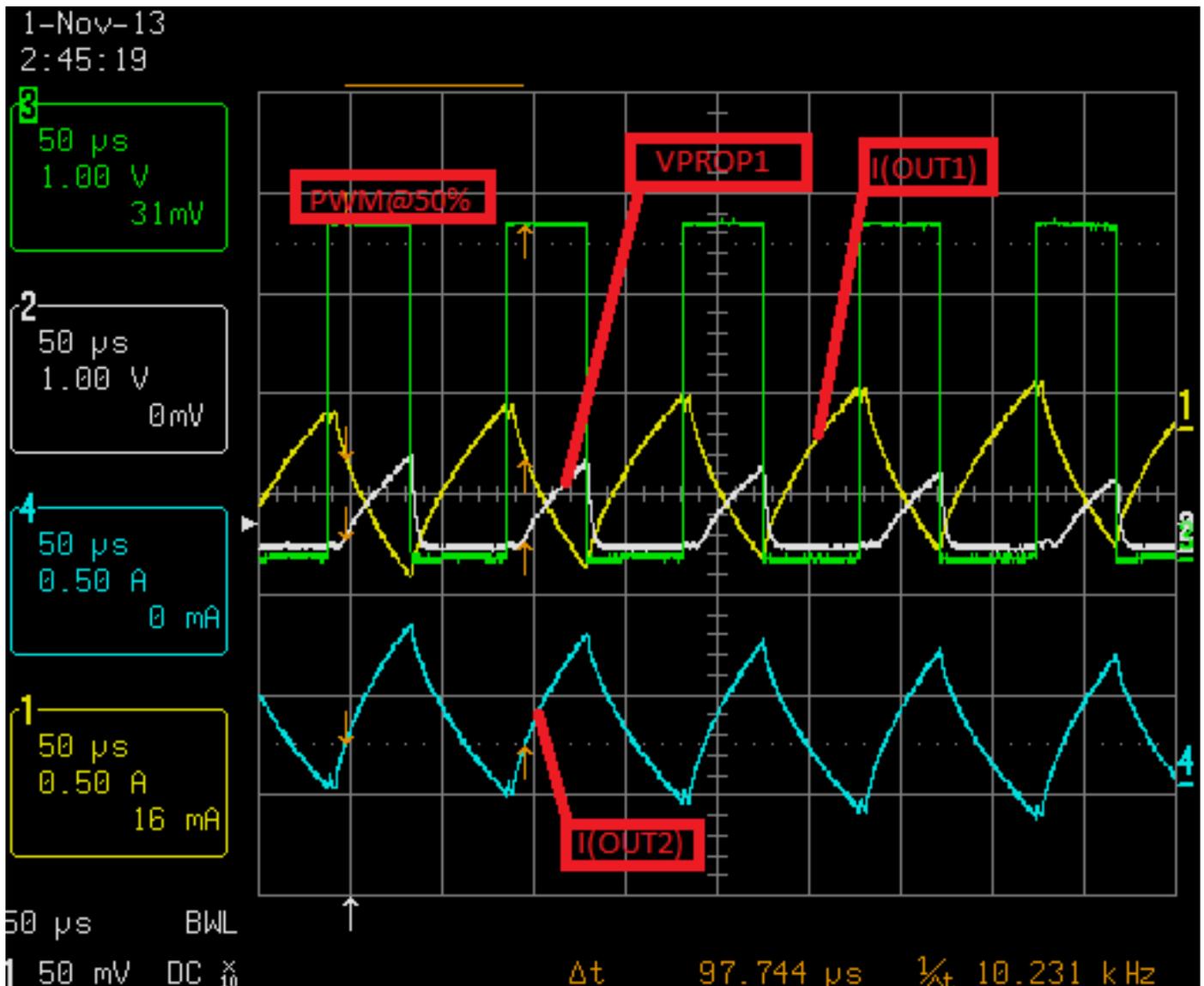
## Section 2. Current proportional output range

A sense resistor of 0.2 ohm is connected to ground for current sensing purposes. The voltage at the VPROP1 is approximately 800mV per captured Waveform. The voltage at the sense pin  $800\text{mV}/5 = 160\text{mV}$ . Thus the current  $I_s$  is calculated to be  $160\text{mV}/0.2\text{ohm} = 800\text{mA}$ .

Referring to  $I(\text{OUT2})$  and  $I(\text{OUT1})$ , the motor currents are very similar to the calculated values.




### Section 3. Motor Voltage versus RPM

This data reflects the non-loaded performance of Anaheim ( BDD-38-63 ) motor configured across OUT1 and OUT2.


The motor's shaft RPM was captured using NEIKO-Laser Photo Tachnometer while varying the motor voltage at VBB terminal and varying the duty cycle by adjusting the potentiometer ( RP1). When the speed reference potentiometer is turned up all the way, 100% duty is attained.

PWM = 10.1KHz	12V @ VBB	20V @ VBB
Min motor current ( 10% dutycycle )	140mA	170mA
Max motor current (100% dutycycle )	630mA	1.1A

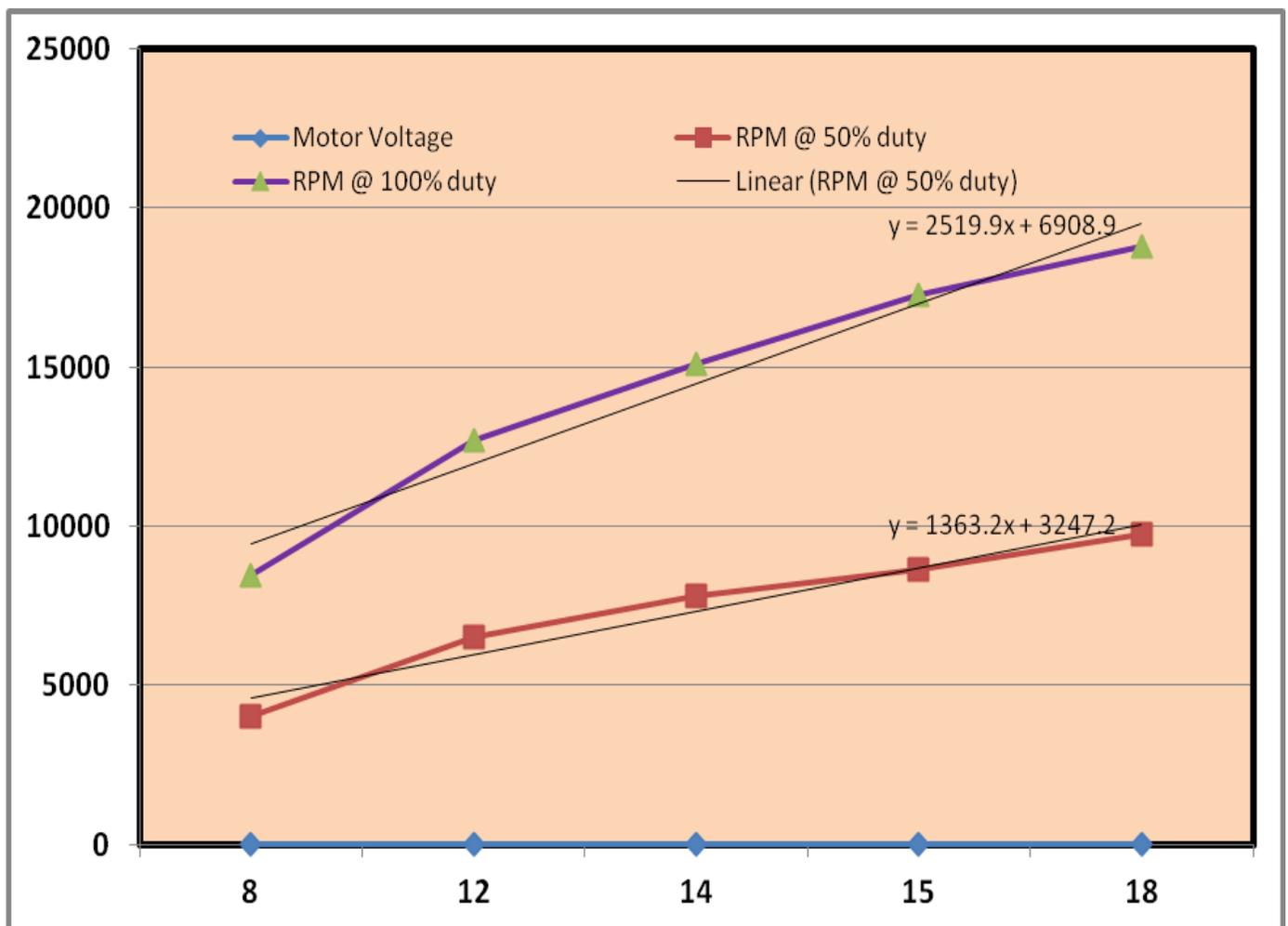
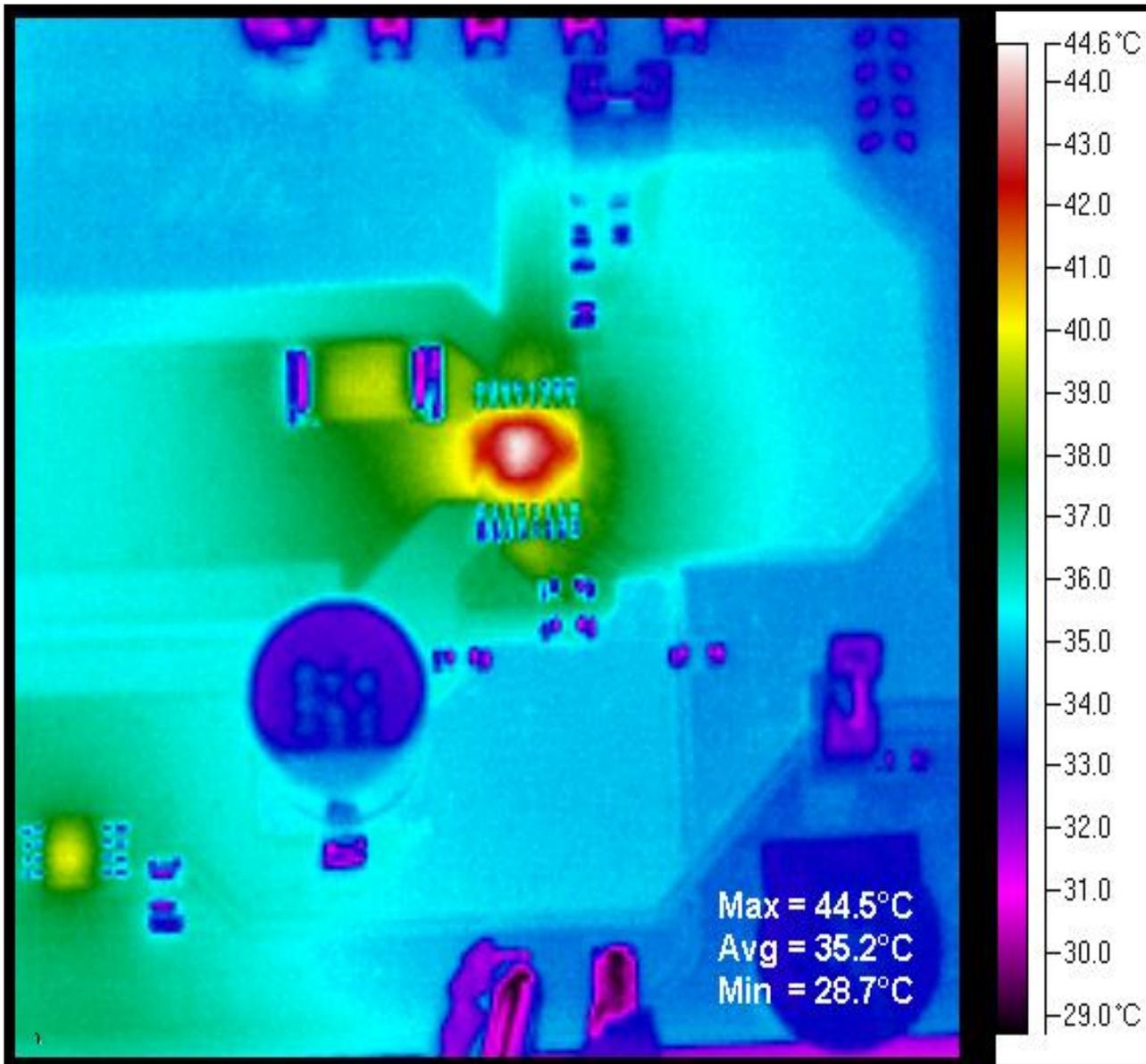
## Section 2. Thermal Image of the device

This data set was collected with the VBB = 20V and  $I_{\text{motor}} = 1.1\text{A}$ .



## Section 2. Thermal Image of the device ( continued )

The IR image was produced in the lab with Fluke –T32 –IR Fusion camera during device operation



## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](#) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated